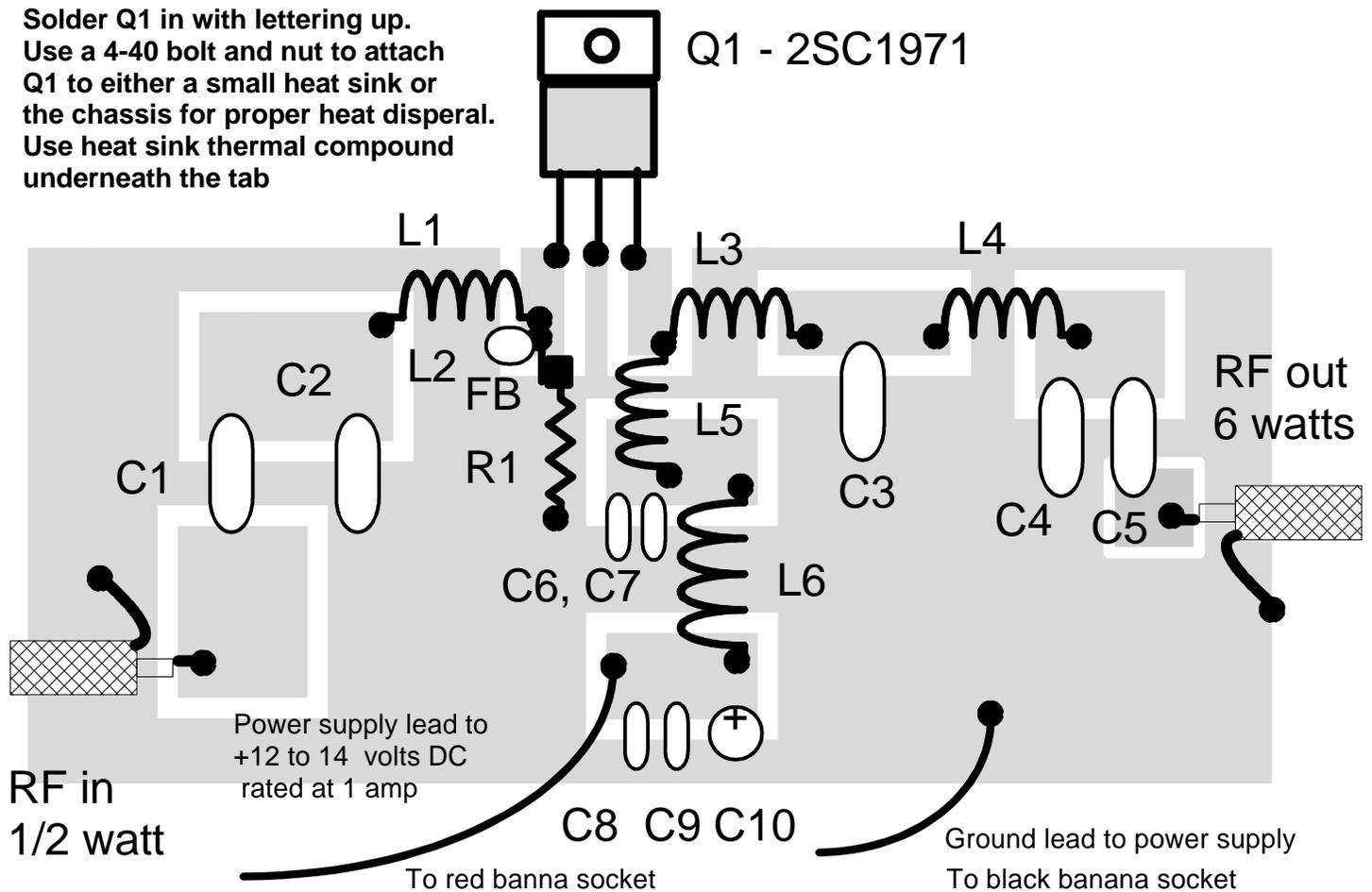


Solder Q1 in with lettering up.  
 Use a 4-40 bolt and nut to attach  
 Q1 to either a small heat sink or  
 the chassis for proper heat dispersal.  
 Use heat sink thermal compound  
 underneath the tab



Q1 - 2SC1971

RF out  
6 watts

RF in  
1/2 watt

Power supply lead to  
+12 to 14 volts DC  
rated at 1 amp

To red banana socket

Ground lead to power supply  
To black banana socket

## Parts List

# 6 Watt RF Amplifier

- C1, C5 - 470 pf mica capacitor
- C2 - 75 pf mica capacitor
- C3 - 39 pf mica capacitor
- C4 - 15 pf mica capacitor
- C6, C8 - .001 uf disc or monolythic capacitor, marked either 102, .001 or 1n
- C7, C9 - .1 uf disc capacitor or monolythic capacitor, marked either 104, .1 or 100n
- C10 - 10 to 22 uf electrolytic (observe correct polarity)
- L1 - 1 turns #18 tinned copper, 1/4 " diameter
- L2 - 1 uh inductor, blue lumpy item
- L3 - 2 turns #18, 1/4" diameter
- L4 - 7/10" # 14, hairpin
- L5, L6 - 5 turns # 20, 1/4 diameter
- R1 - 56 ohm resistor with ferrite bead over lead at the base end of Q1
- Q1 - 2SC1971 RF transistor
- Misc - RG174 coax, hookup wire, SO239 sockets (2), 4-40 nuts and bolts (4 each) ferrite bead, banana sockets & plugs (red/black 2 ea.) and solder lugs

Assemble by soldering the components to the pads indicated. Keep coil, resistor and capacitor leads as short as possible. The coils should be 3/16"-1/4" above the board and separate turns by one wire diameter, bend lead to form a little mounting foot for soldering to the circuit board. Tuning & power output are affected by the distance between the coil turns, you can make fine adjustments by either spreading or compressing the coil slightly. The area surrounding the pads is ground, C2, C3, C4 & C6-C10, L2 and R1 are soldered at one end to ground as well as the shield braid on the coax cables. Bolt Q1 to a small heat sink or the chassis with heat sink thermal compound or gray thermal pad underneath the tab. With an input level of 200-500 mw you should see an output of 5-6 watts. Be sure to have a proper dummy load (50 ohms) or tuned antenna connected to the output, doing otherwise will likely destroy the transistor.

